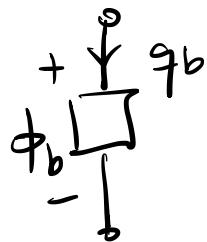


# Fundamentals of circuit

## Quantisation.


Lump element:




$$\phi_b = \int_0^t dz v(z)$$

$$q_b = \int_0^t dz i(z)$$


inductors

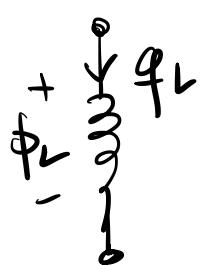

capacitors .

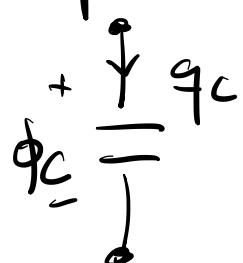

# The node-flux method:

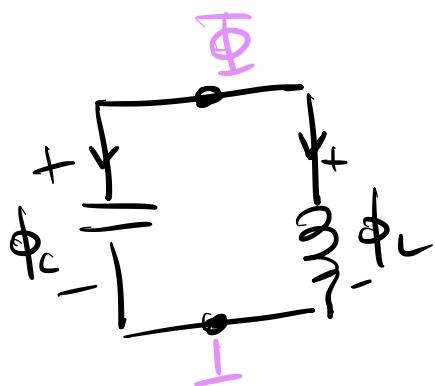

Only solve the KVL!

$$d\phi_C = d\phi_L = d\bar{\Phi}$$

$$\ast = \frac{C \dot{\phi}_C^2}{2} - \frac{\dot{\phi}_L^2}{2L}$$

(Integrate KVL constraints)

$$L = C \frac{\dot{\bar{\Phi}}^2}{2} - \frac{(\dot{\bar{\Phi}} + k)^2}{2L}$$

$$\downarrow Q = C \dot{\bar{\Phi}} \quad \{ \dot{\phi}, Q \} = 1$$

$$H = \frac{Q^2}{2C} + \frac{(\dot{\bar{\Phi}} + k)^2}{2L}$$

if constant; can  
be gauged away.




$$\phi_C = \bar{\Phi}$$


$$\phi_L = \bar{\Phi} + \frac{k^2}{2L}$$

↑  
constant.


## Lump element:

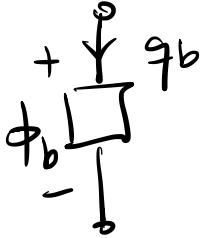

inductors

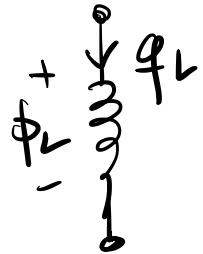

capacitors .

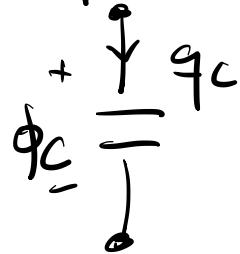

Contributions  
to energy  
functions:

$$\frac{1}{2} \dot{\phi}_L q_L - \frac{\dot{\phi}_L^2}{2L}$$

$$\frac{1}{2} \dot{q}_C \phi_C - \frac{\dot{q}_C^2}{2C}$$

Kirchhoff's laws:  
(constraints)

$$\left\{ \begin{array}{l} \text{KVL: } \vec{F}_{\text{loop}} d\vec{\phi} = 0 \\ \text{KCL: } \vec{F}_{\text{cut set}} d\vec{q} = 0 \end{array} \right.$$

$$\vec{F} d\vec{z} = \begin{pmatrix} \vec{F}_{\text{loop}} & 0 \\ 0 & \vec{F}_{\text{cut}} \end{pmatrix} \begin{pmatrix} d\vec{\phi} \\ d\vec{q} \end{pmatrix} = 0$$

$$\vec{F} \vec{k} = 0$$


$\hookrightarrow$  Basis of

fluxes and charges .

$$K = K_{\text{loop}} \oplus K_{\text{cut}}$$

Something more  
on the basis .

### Example 1 LC circuit.

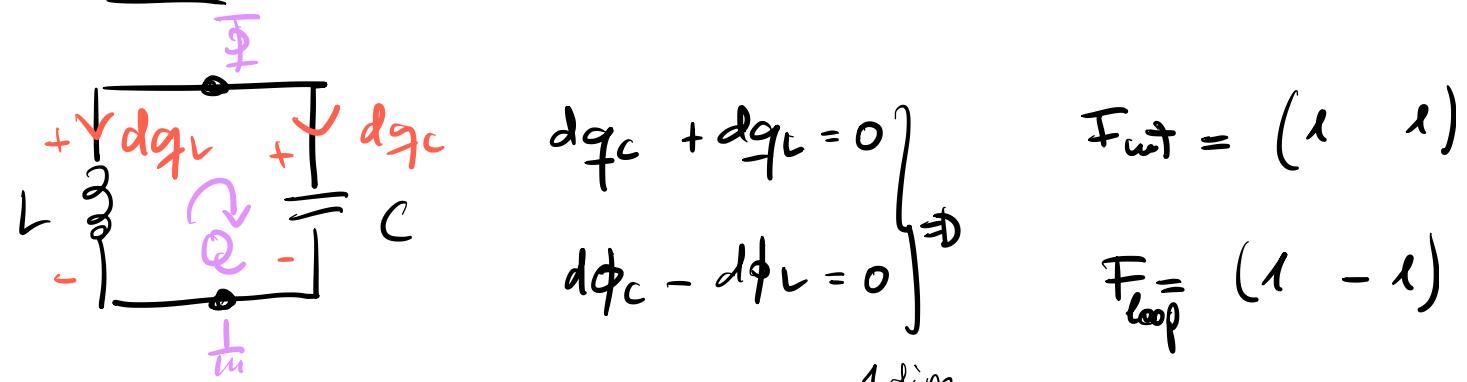

$$F_{wt} K_{wt} = 0$$

$$K_{wt} = \left\{ \begin{pmatrix} 1 \\ -1 \end{pmatrix} \right\}^{\text{1 dim}}$$

$$F_{loop} K_{loop} = 0 \quad K_{loop} = \left\{ \begin{pmatrix} 1 \\ 1 \end{pmatrix} \right\}^{\text{1 dim}}$$

$$\begin{pmatrix} \frac{dq_C}{dt} \\ \frac{dq_L}{dt} \end{pmatrix} = \boxed{dQ} \begin{pmatrix} 1 \\ -1 \end{pmatrix}$$

$$\begin{pmatrix} \frac{d\phi_C}{dt} \\ \frac{d\phi_L}{dt} \end{pmatrix} = \boxed{d\Phi} \begin{pmatrix} 1 \\ 1 \end{pmatrix}$$

We construct the energy function that will become a h.

$$* = \frac{1}{2} (\dot{q}_C \dot{\phi}_C + \dot{\phi}_L \dot{q}_L) - \left( \frac{q_C^2}{2C} + \frac{\phi_L^2}{2L} \right)$$

(integrate Kirchhoff's laws:


$$L = \frac{1}{2} \underbrace{(\dot{Q}\dot{\Phi} - \dot{\Phi}\dot{Q})}_{\circ} - \left( \frac{Q^2}{2C} + \frac{\Phi^2}{2L} \right)$$

$$\frac{1}{2} \begin{pmatrix} Q \\ \Phi \end{pmatrix}^T \begin{pmatrix} 1 & -1 \\ -1 & 1 \end{pmatrix} \begin{pmatrix} Q \\ \Phi \end{pmatrix}$$

$$z^T W^{-1} z = \{z, z^T\} \leftrightarrow \text{Poisson bracket} - \hat{S.C.R.}$$

## Kirchhoff's Constraints

Example 2:

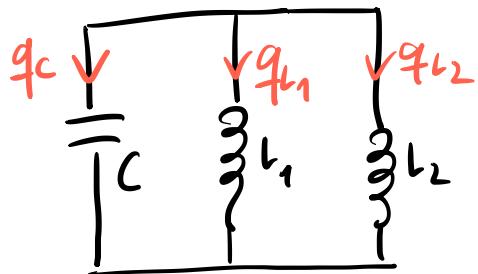

$$\left\{ \begin{array}{l} dq_C + dq_{L_1} + dq_{L_2} = 0 \quad 1 \text{ eq.} \rightarrow 2 Q_s \\ d\phi_C = d\phi_{L_1} = d\phi_{L_2} \quad 2 \text{ eqs.} \rightarrow 1 \Phi \end{array} \right.$$

$$2 \times 3 \text{ variables} - 3 \text{ eqs.} = \boxed{3}$$

$$F_{wt} = \begin{pmatrix} 1 & 1 & 1 \end{pmatrix}$$

$$F_{loop} = \begin{pmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \end{pmatrix}$$

$$\dim \ker(F_{wt}) = 2$$

$$\dim \ker(F_{loop}) = 1$$


A basis for fluxes and charges:

$$dq_C = dQ_1$$

$$dq_{L_2} = dQ_2$$

$$dq_{L_1} = -d(Q_1 + Q_2)$$
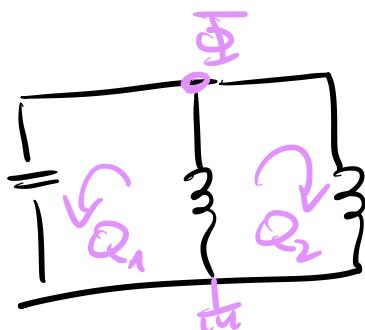
$$d\phi_C = d\phi_{L_1} = d\phi_{L_2} = d\Phi$$



Energy function:

$$* = \frac{1}{2} \left( q_C \dot{\phi}_C + \phi_{L_1} \dot{q}_{L_1} + \phi_{L_2} \dot{q}_{L_2} \right) - \left( \frac{q_C^2}{2C} + \frac{\dot{\phi}_{L_1}^2}{2L_1} + \frac{\dot{\phi}_{L_2}^2}{2L_2} \right)$$

↓  
Integrate constraints.

$$L = \frac{1}{2} (\dot{Q}_1 \dot{\Phi} + \dot{\Phi} (-\dot{Q}_1 - \dot{Q}_2) + \dot{\Phi} \cancel{(\dot{Q}_2)})$$

$$\begin{aligned} & - \left( \frac{Q_1^2}{2C} + \frac{\dot{\Phi}^2}{2} \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \right) \xrightarrow{\text{Parallel summation rule.}} \\ & = \frac{1}{2} (Q_1 \dot{\Phi} - \dot{\Phi} Q_1) - H \\ & \quad \underbrace{\dot{W} = (\Sigma, \mathcal{I})^{-1}}_{\text{rule.}} \end{aligned}$$


---

The first order term in the Lagrangian is associated with a 2-form.

$$L_W = \frac{1}{2} (q_C \dot{\phi}_C + \dot{\phi}_L \dot{q}_L + \dots)$$



$$W = \frac{1}{2} (dq_C \wedge d\phi_C + d\phi_L \wedge dq_L + \dots)$$

$$d\alpha_1 \wedge d\alpha_2 = -d\alpha_2 \wedge d\alpha_1$$